

## Verilog Code

```
module full_adder(

    input A, B, Cin,

    output Sum, Cout

);

    assign Sum = A ^ B ^ Cin;    // XOR operation

    assign Cout = (A & B) | ((A ^ B) & Cin);

endmodule
```

## Test Bench Code

```
module tb_adder;

    reg A, B, Cin;

    wire Sum, Cout;

    // Instantiate Full Adder

    full_adder dut (

        .A(A),

        .B(B),

        .Cin(Cin),

        .Sum(Sum),

        .Cout(Cout)

    );

    initial begin

        A=0; B=0; Cin=0; #10;

        $display("A=%b B=%b Cin=%b -> Sum=%b Cout=%b", A,B,Cin,Sum,Cout);

        A=0; B=0; Cin=1; #10;

        $display("A=%b B=%b Cin=%b -> Sum=%b Cout=%b", A,B,Cin,Sum,Cout);

        A=0; B=1; Cin=0; #10;
```

```

$display("A=%b B=%b Cin=%b -> Sum=%b Cout=%b", A,B,Cin,Sum,Cout);

A=1; B=1; Cin=1; #10;

$display("A=%b B=%b Cin=%b -> Sum=%b Cout=%b", A,B,Cin,Sum,Cout);


$finish;

end

endmodule

```

## Circuit

 

## Truth Table

Input			Output	
A	B	Cin	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

## Output Wave Forms

